

Symulacja obwodowa modelu o zredukowanym rzędzie ROM (ANSYS Q3D) w środowisku MATLAB_Simulink



PUBLIC

Agenda

1

About us and
Rockwell Automation

2

Problem
description

3

Equivalent DC link
capacitor model

4

RLCG model of
laminated busbars
ANSYS simulation

5

Multi-physics
circuit simulations
MATLAB/Simulink

6

ROM Model
validation

7

DC/AC inverter
simulations with
busbar ROM model

8

Summary & future
research



1. About us and Rockwell Automation



Rockwell Automation – company introduction



Dr inż. Wojciech Jurczak

Power electronics architect

Low voltage drives



Mgr inż. Dawid Stawiarski

Power electronics engineer

Low voltage drives



Mgr inż. Kamil Zygmunt

Simulation engineer

Low voltage drives



expanding **human possibility**[®]

2800+ employees in Poland



PUBLIC

AT A GLANCE



Rockwell Automation

Our strategy is to bring The Connected Enterprise to life.

We integrate control and information across the enterprise to help industrial companies and their people be more productive and sustainable.

\$9.1B

FISCAL 2023 SALES

29,000

EMPLOYEES

100+

COUNTRIES

ABOVE-MARKET GROWTH | PRODUCTIVITY | INTELLECTUAL CAPITAL >>> VALUE CREATION



PUBLIC

1. About us and Rockwell Automation

Low Voltage Drives



Premium



Standard



Compact

PowerFlex 755TS & 755TM
UL/IEC: 400/690 up to 4000A

PowerFlex® Medium Voltage Drives




PowerFlex 6000 & 7000
UL/IEC: 2.3kV - 11kV up to 680A
UL/IEC: 2.3kV - 6.6kV up to 720A

Programming & communication




DeviceNet
ControlNet
ProfiNet
ProfiBus

2. Problem description

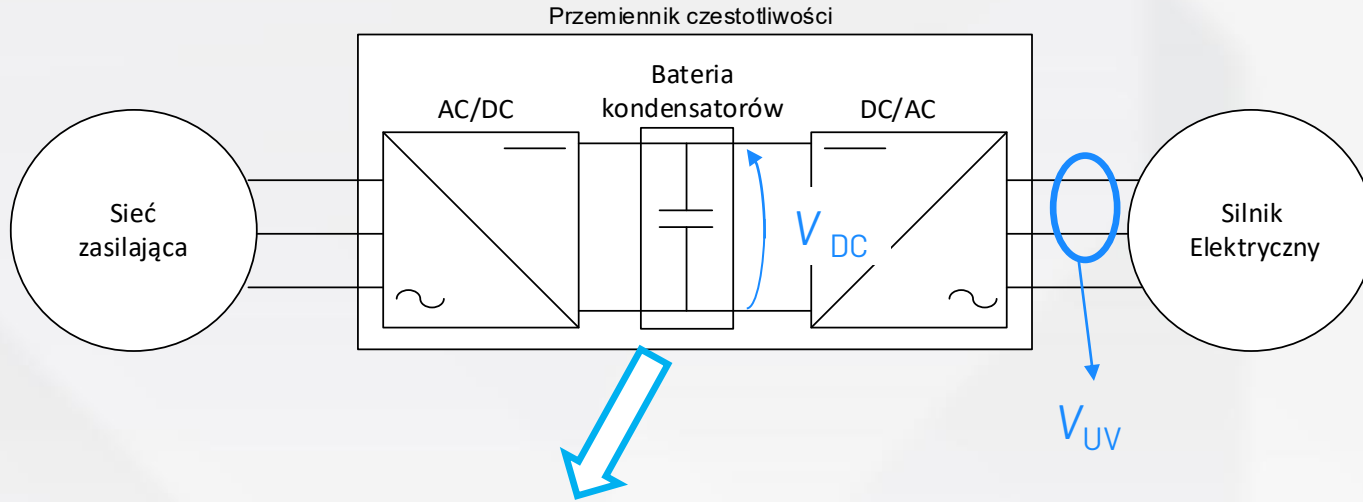


DC capacitor bank requirements

- **Capacitance vs V_{DC} ripples**

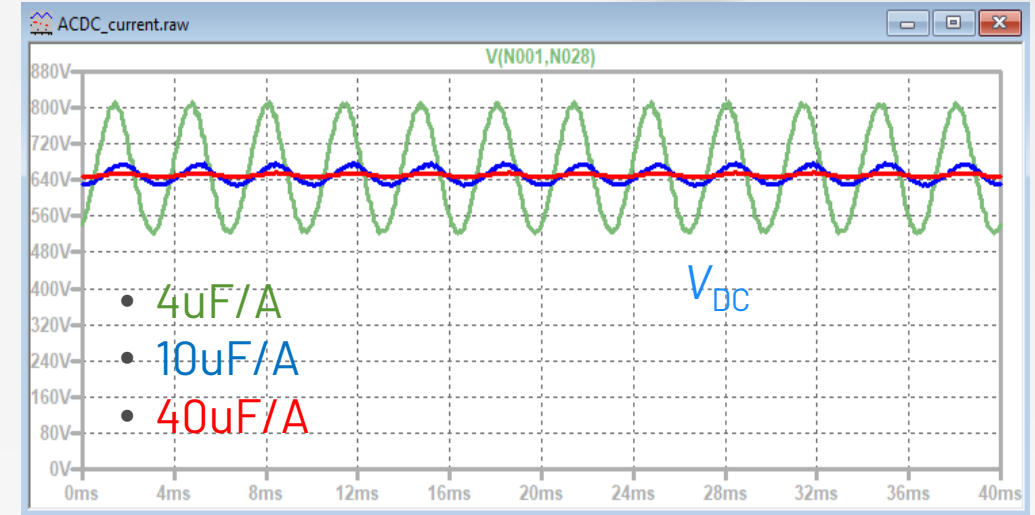


- **4uF/A**

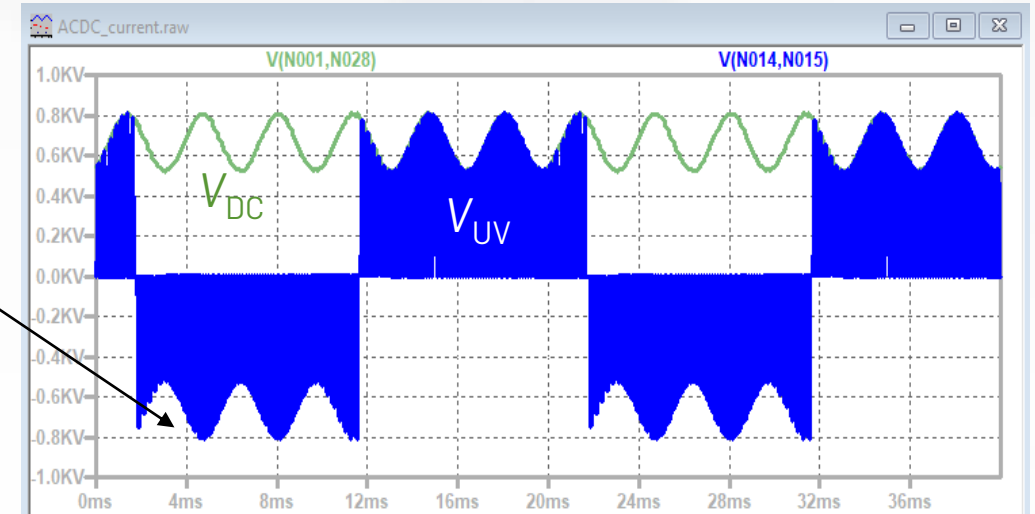


1. High V_{DC} ripples
2. Output voltage ripples
3. Motor torque ripples

Cost-Benefits Analysis

 

2. Problem description

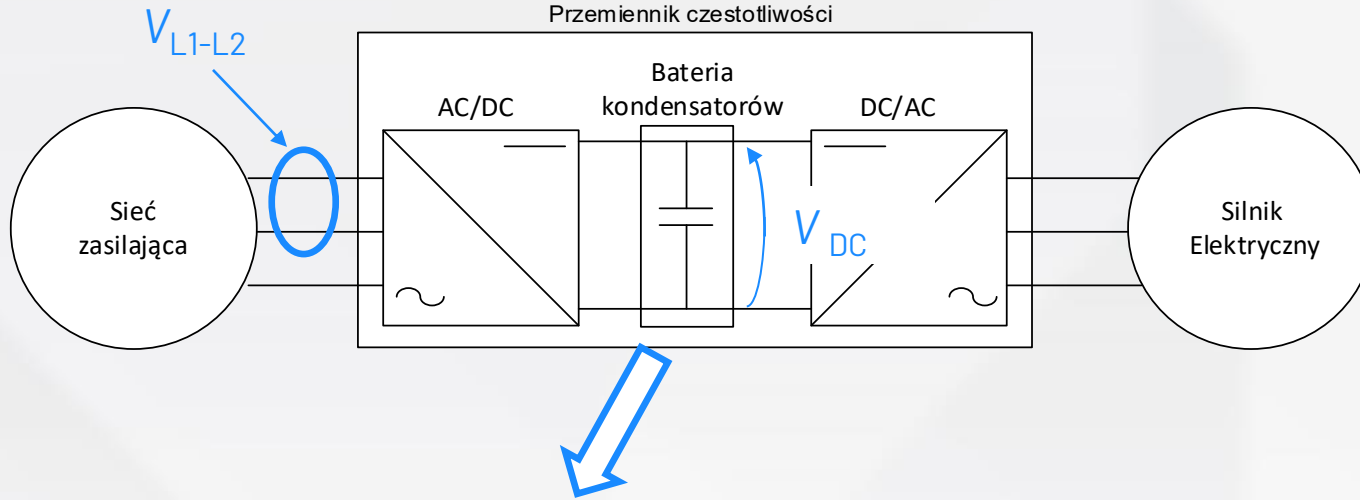

For 400/480 V_{AC} drives

- $564/677 V_{DC}$ Normal operation
- Up to 800V during motor deceleration


For 600/690 V_{AC} drives

- $846/973 V_{DC}$ Normal operation
- Up to 1100V during motor deceleration

$$V_{DC} = \sqrt{2} \cdot V_{L1-L2}$$

DC capacitor bank requirements

 - Capacitance vs V_{DC} ripples
- **High DC voltage operation**






Series connection needed

Comparison of the parameters of the different aluminum electrolytic capacitors types

Electrolyte	Capacitance range	Rated voltage range	Typical ESR ¹⁾ 100 kHz, 20 °C	Typical ripple current ¹⁾ 100 kHz, 105 °C	Leakage current ¹⁾ after 2 minutes at 10 V
Non-solid borax or organic	0.1 μF–2.7 F	4–630 V	800 mΩ	130 mA	< 10 μA
Non-solid water-based	1–18000 μF	4–100 V	360 mΩ	240 mA	10 μA
Solid manganese dioxide	0.1–1500 μF	6.3–40 V ^[8]	400 mΩ	620 mA	12 μA
Solid conducting polymer	2.2–2700 μF	2–125 V ^[9]	25 mΩ	2.5 A	240 μA
Solid and non-solid hybrid electrolyte	6.8–1000 μF	6.3–125 V ^[10]	40 mΩ	1.5 A	100 μA

*source: https://en.wikipedia.org/wiki/Aluminum_electrolytic_capacitor


2. Problem description

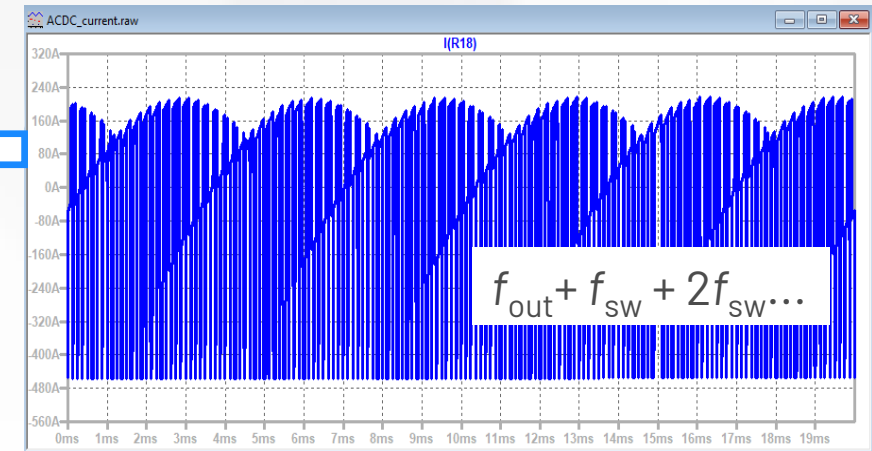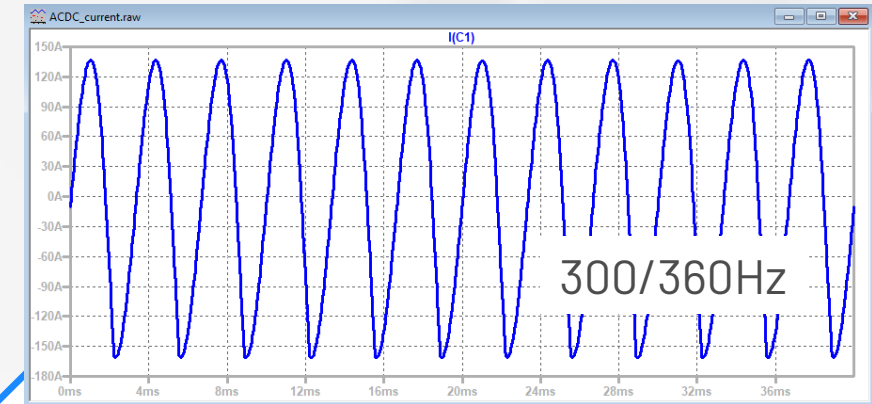 


DC capacitor bank requirements

- Capacitance vs V_{DC} ripples
- High DC voltage operation
- **Handle LF and HF currents**

$$I_c \sim 0.6 I_{out}$$

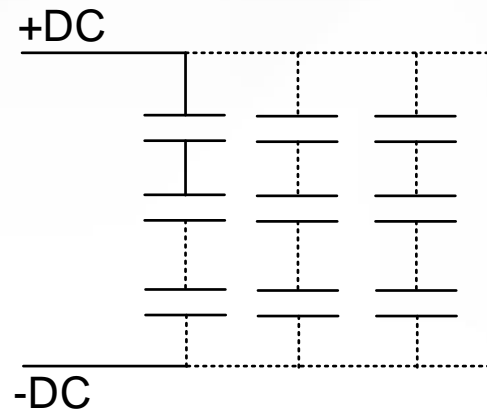

2. Problem description

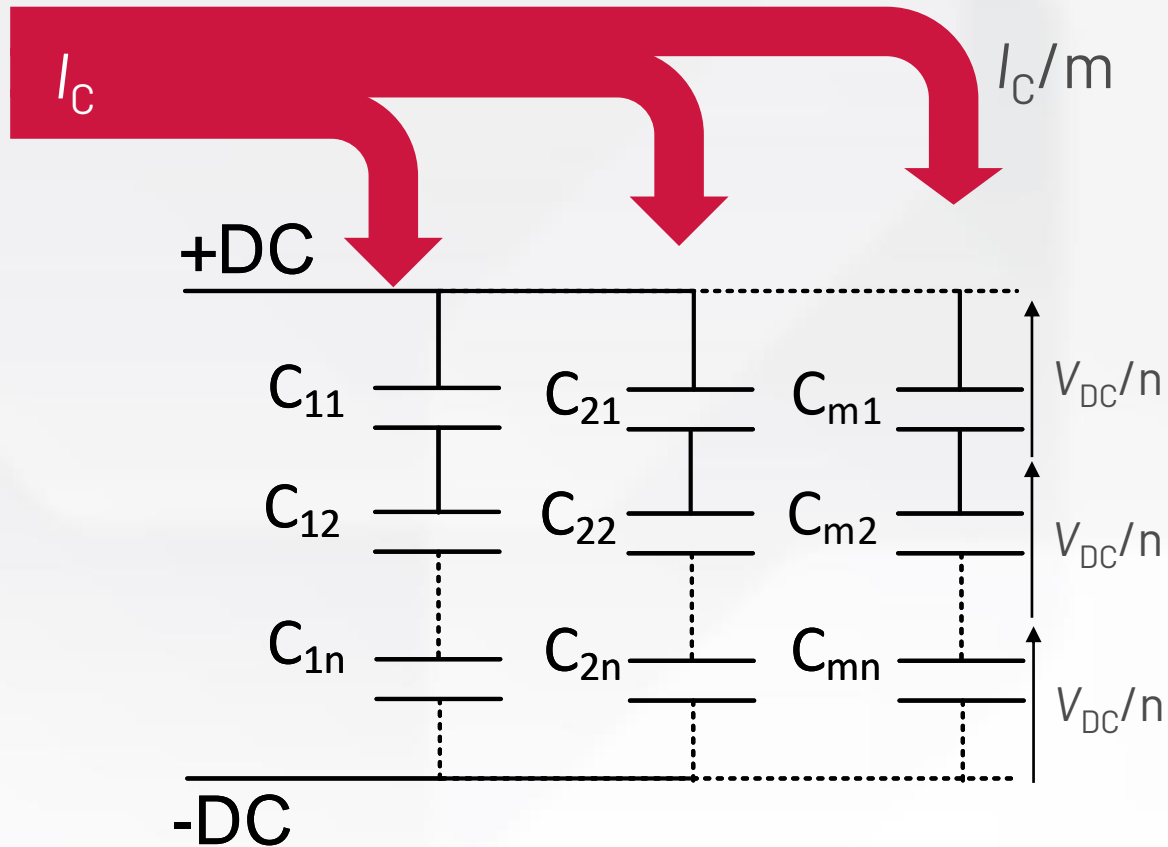

Series connection:

Voltage balancing required:

- easy to maintain (balancing resistors).


Parallel connection:

Current sharing/power losses:

- hard to predict and measure,
- parasitic resistances & inductances,
- capacitor parameters,
- mechanical connections.


Setup with $n=2$ and $m=4$ was analyzed

 3. Equivalent DC link capacitor model (ESR & ESL)




ESL - equivalent series inductance

ESR - equivalent series resistance

 

C_{DC} - Capacitor capacitance

 



E & (I_{CR})




T1




T2 + D

 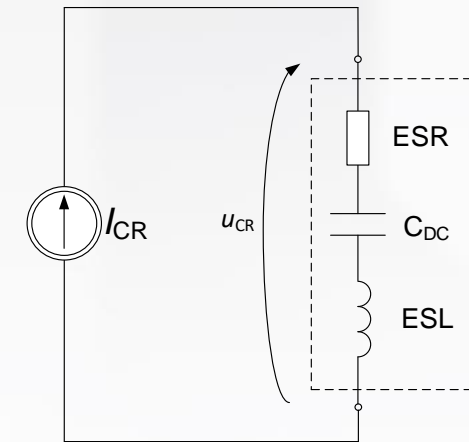

 3. Equivalent DC link capacitor model (ESR & ESL)



 Scope waveforms for ESR and ESL measurement of C_1



$$\Delta U_{ESL} = 0.42 \text{ V}$$

$$\Delta I_C = 9.58 \text{ A}$$

$$\Delta t = 1.5 \text{ } \mu\text{s}$$

$$ESL = \frac{\Delta U_{ESL}}{\frac{\Delta I_C}{\Delta t}} = 65.77 \text{ nH}$$



$$\Delta U_{ESR} = 1.47 \text{ V}$$

$$I_C = 83.2 \text{ A}$$

$$ESR = \frac{\Delta U_{ESR}}{I_C(t_x)} = 17.66 \text{ m}\Omega$$

  3. Equivalent DC link capacitor model (C_{DC})

Scope waveforms for C_{DC} capacitance measurement of C_1



$$I_{CR} = 148.4 \text{ mA}$$

$$\Delta t = 1.87 \text{ s}$$

$$\Delta U_{CE} = 74.26 \text{ V}$$

$$C_{DC} = \frac{I_{CR}}{\frac{\Delta U_{CR}}{\Delta t}} = 3.74 \text{ mF}$$

3. Equivalent DC link capacitor model (C_{DC})

Test results for measured capacitors

	C [mF]	ESL [nH]	ESR [mΩ]
C1	3,74	65,77	17,66
C2	3,82	61,86	17,04
C3	3,90	55,56	17,35
C4	3,79	64,93	17,35
C5	3,91	57,02	16,72
C6	3,84	59,28	16,88
C7	3,98	56,99	16,72
C8	3,81	55,75	17,04


Datasheet

$C = 4.1\text{mF (+/-20\%)}$

$\text{ESR}_{\text{max}} = 20 \text{ m}\Omega$

$\text{ESL}_{\text{max}} = 50 \text{ nH}$




4. Laminated busbars ROM model

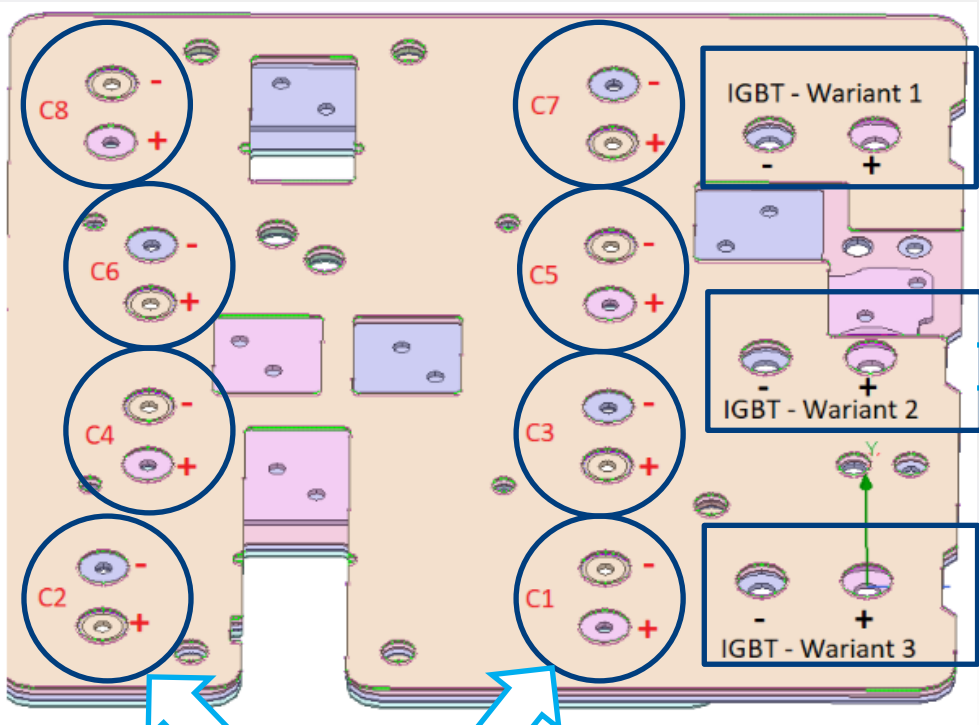




Capacitor placement



IGBT placement

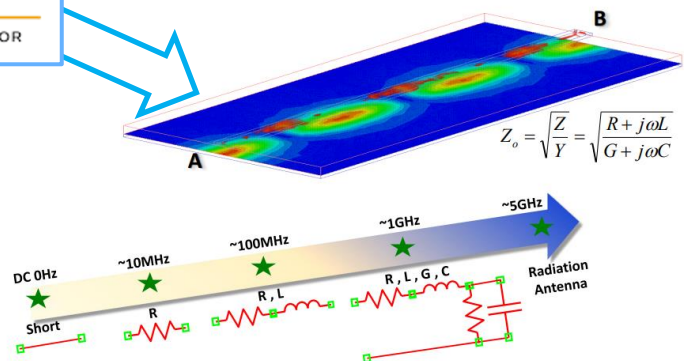  

4. Laminated busbars ROM model

   

Big impact of laminated busbars design for current flow distribution




5. Multi-physics simulations - model export



.cir file

ANSYS Q3D

Extraction of RLCG parasitic parameters.

 


MATLAB Scripts

Generation Simscape model from CiR file

```

.subckt Variant_1_half 1 2 3 4 5 6 7 8 9 10 11 12 13 14 15 16 17 18
+ 23 24 25 26 27 28 29 30 31 32 33 34
V1 1 35 dc 0.0
V2 2 36 dc 0.0
V3 3 37 dc 0.0
V4 4 38 dc 0.0
V5 5 39 dc 0.0
V6 6 40 dc 0.0
V7 7 41 dc 0.0
V8 8 42 dc 0.0
V9 9 43 dc 0.0
V10 10 44 dc 0.0
V11 11 45 dc 0.0
V12 12 46 dc 0.0
V13 13 47 dc 0.0
V14 14 48 dc 0.0
V15 15 49 dc 0.0
V16 16 50 dc 0.0
V17 17 51 dc 0.0
R1 35 52 2.549731648023e-05
R2 36 53 4.38041411191e-05
R3 37 54 1.93964491272e-05
R4 38 55 2.39165563367e-05
R5 39 56 2.24001356977e-06
R6 40 57 2.56144775532e-05
R7 41 58 8.29661459903e-06
R8 42 59 3.29168773971e-05
R9 43 60 4.58835254491e-05
R10 44 61 1.95571916746e-05
R11 45 62 2.88773239354e-05
R12 46 63 1.04887419661e-05
R13 47 64 8.31371029309e-05
R14 48 65 7.88022466381e-05
R15 49 66 6.43035043551e-05
R16 50 67 9.40803089212e-05
R17 51 68 1.27501083746e-06
F1_2 52 35 V2 0.508074
F1_3 52 35 V3 0.659486
F1_4 52 35 V4 0.452973
F1_5 52 35 V5 -0.00631487
F1_6 52 35 V6 0.407966
F1_7 52 35 V7 0.0778246
F1_8 52 35 V8 0.312353
F1_9 52 35 V9 0.0477824
F1_10 52 35 V10 0.0821684

```

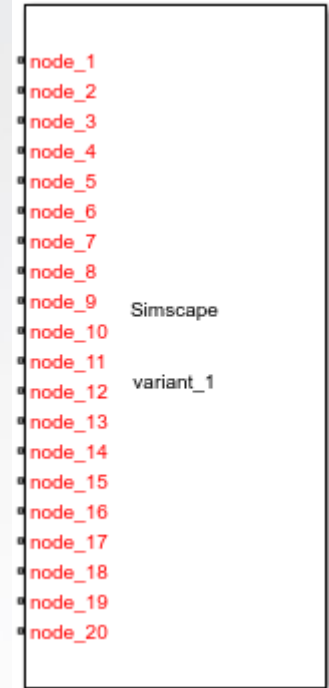


Thank You
FOR YOUR
SUPPORT




Oprogramowanie
Naukowo-Techniczne
sp. z o.o.



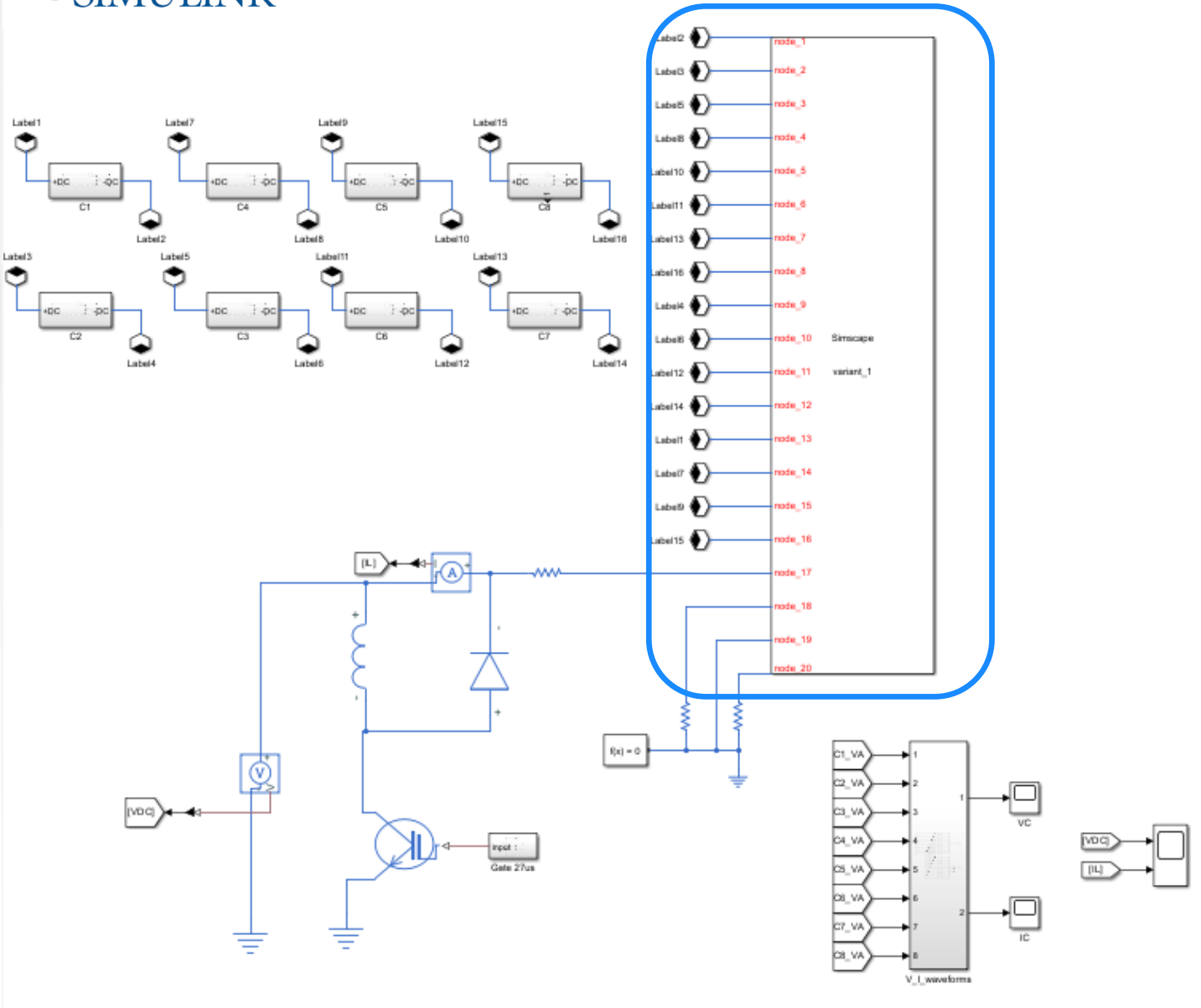5. Multi-physics circuit simulations – pulse test





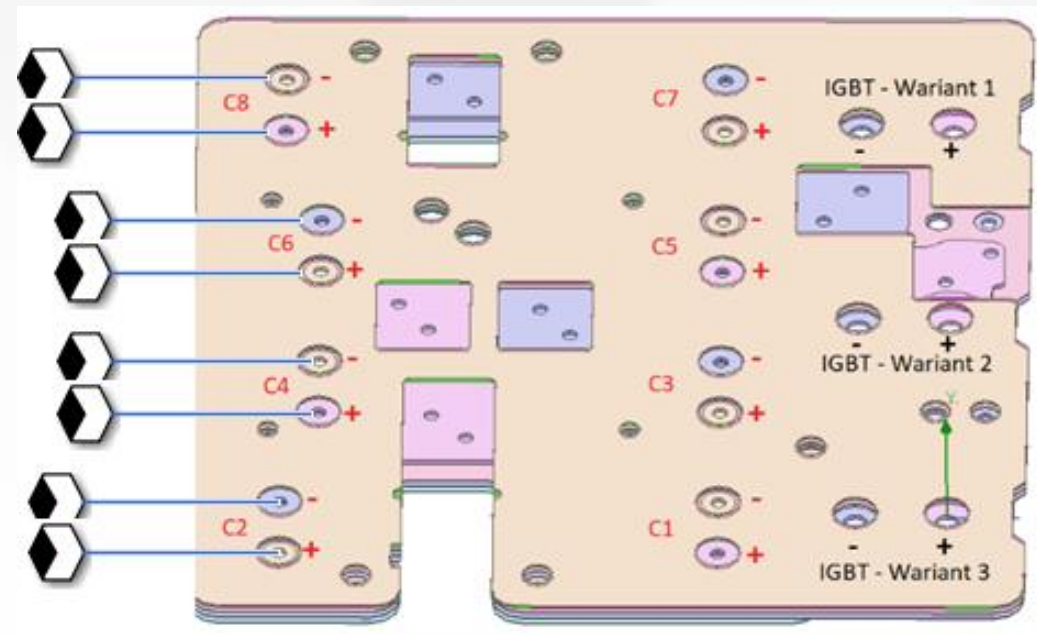1. Busbars Q3D model (ROM model)
2. Capacitors RLC models
3. IGBT + Inductor



5. Multi-physics circuit simulations – pulse test

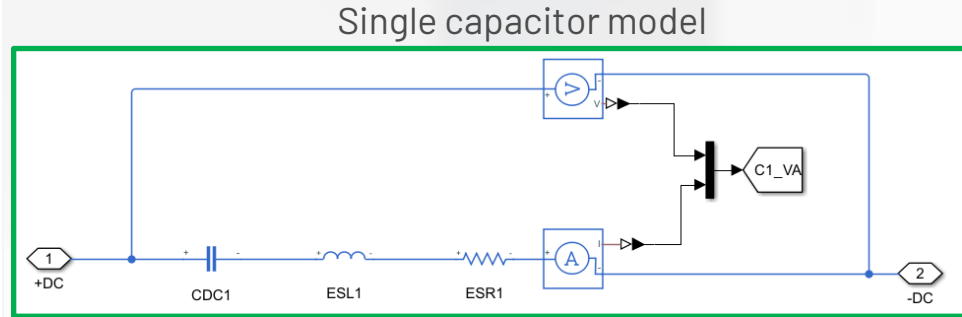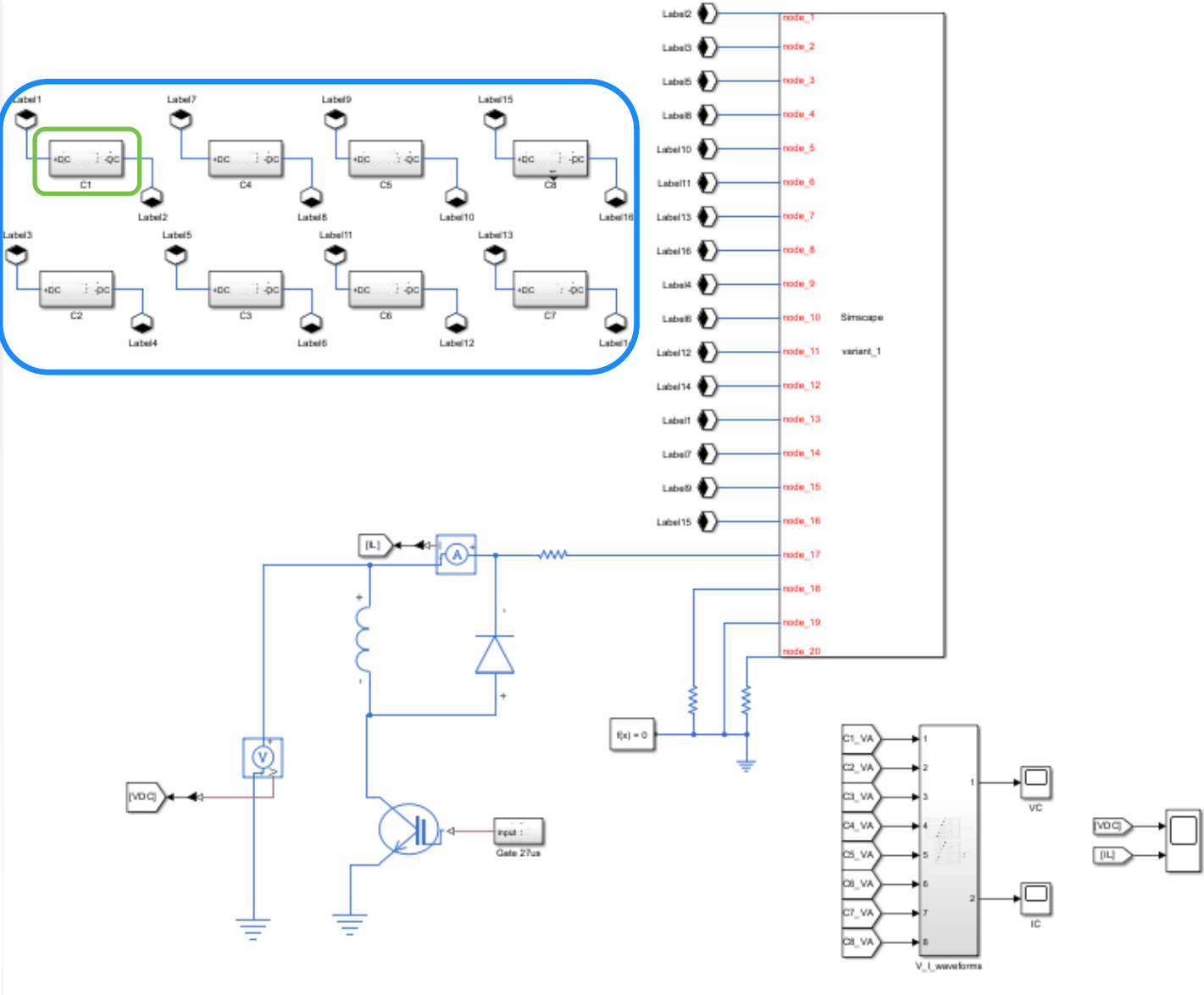
- 1. Busbars Q3D model (ROM model)
- 2. Capacitors RLC models
- 3. IGBT + Inductor



8 capacitors
575 V/4.1 mF



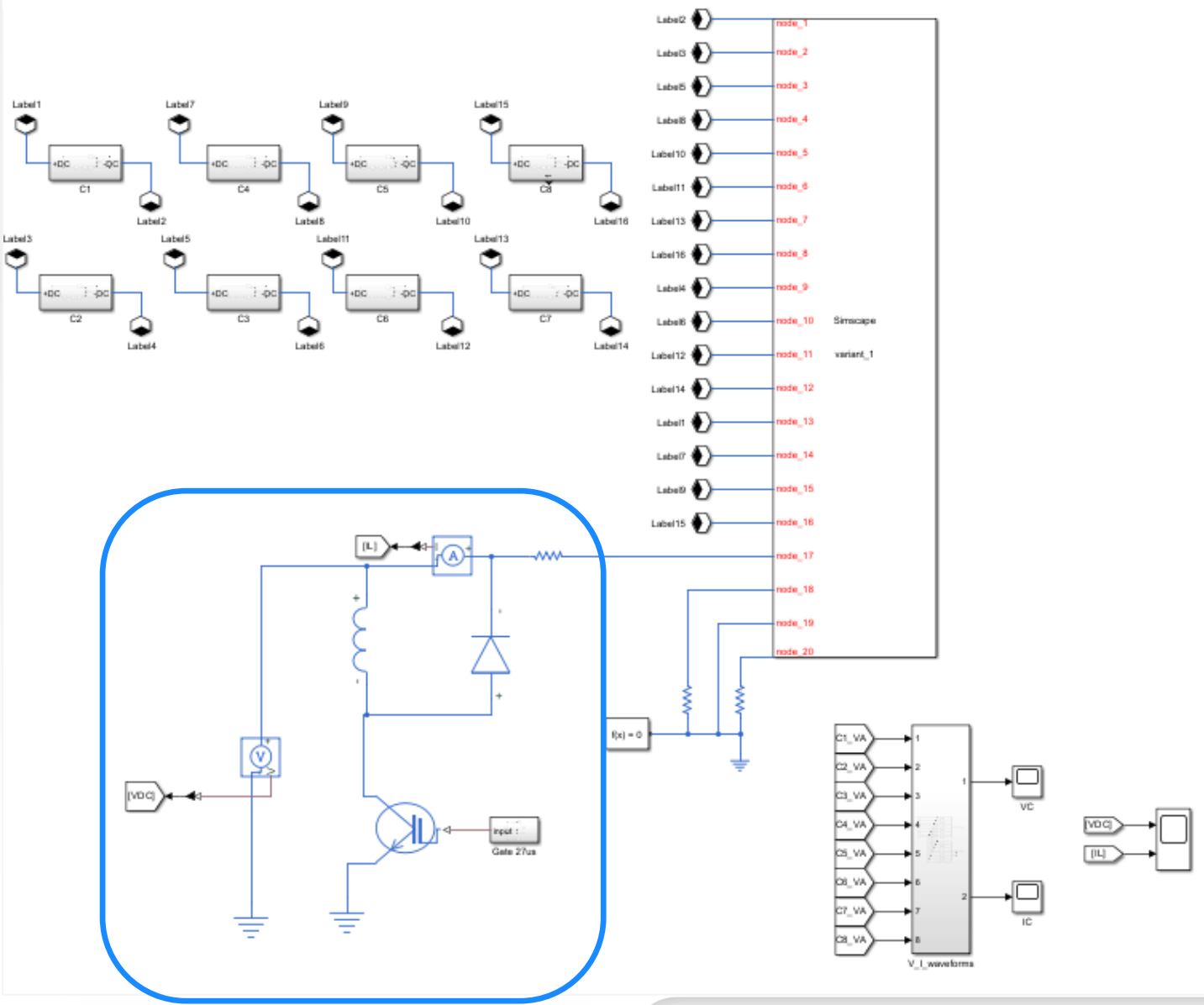5. Multi-physics circuit simulations – pulse test







1. Busbars Q3D model (ROM model)
2. Capacitors RLC models
3. IGBT + Inductor

1.2kV/1.2kA




25mm²
~6 turns
d ~35-50cm

5. Multi-physics circuit simulations

 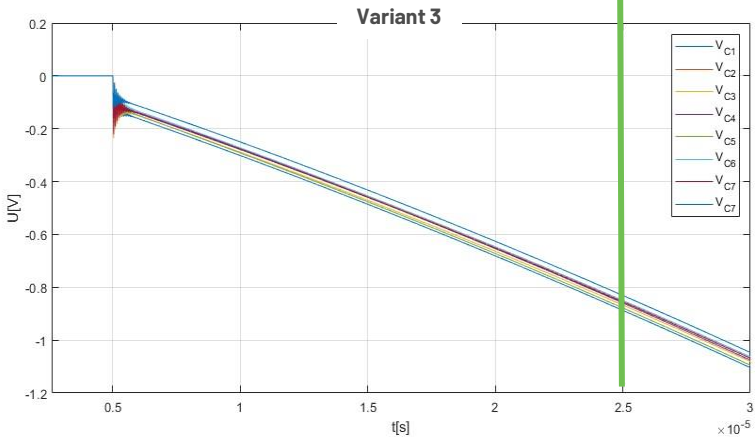 
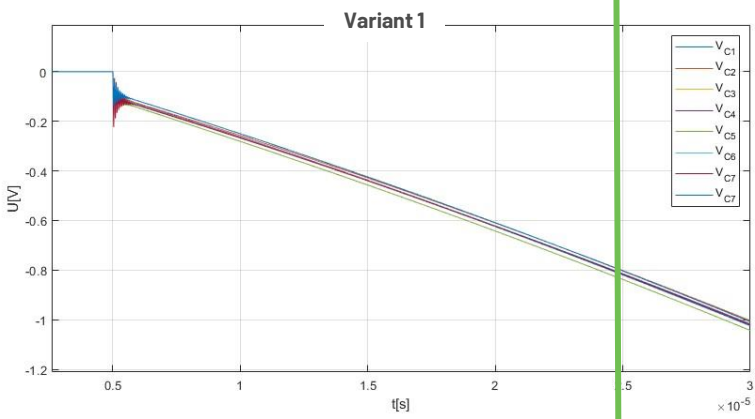


	Variant 1	Variant 2	Variant 3
U_{C1} [mV]	764	797	810
U_{C2} [mV]	752	774	783
U_{C3} [mV]	761	788	791
U_{C4} [mV]	763	787	793
U_{C5} [mV]	777	796	800
U_{C6} [mV]	759	781	787
U_{C7} [mV]	759	770	790
U_{C8} [mV]	755	772	780



	C [mF]	ESL [nH]	ESR [mΩ]
C1	3,74	65,77	17,66
C2	3,82	61,86	17,04
C3	3,90	55,56	17,35
C4	3,79	64,93	17,35
C5	3,91	57,02	16,72
C6	3,84	59,28	16,88
C7	3,98	56,99	16,72
C8	3,81	55,75	17,04

 

6. ROM Model validation – test setup

  


6. ROM Model validation – test results

 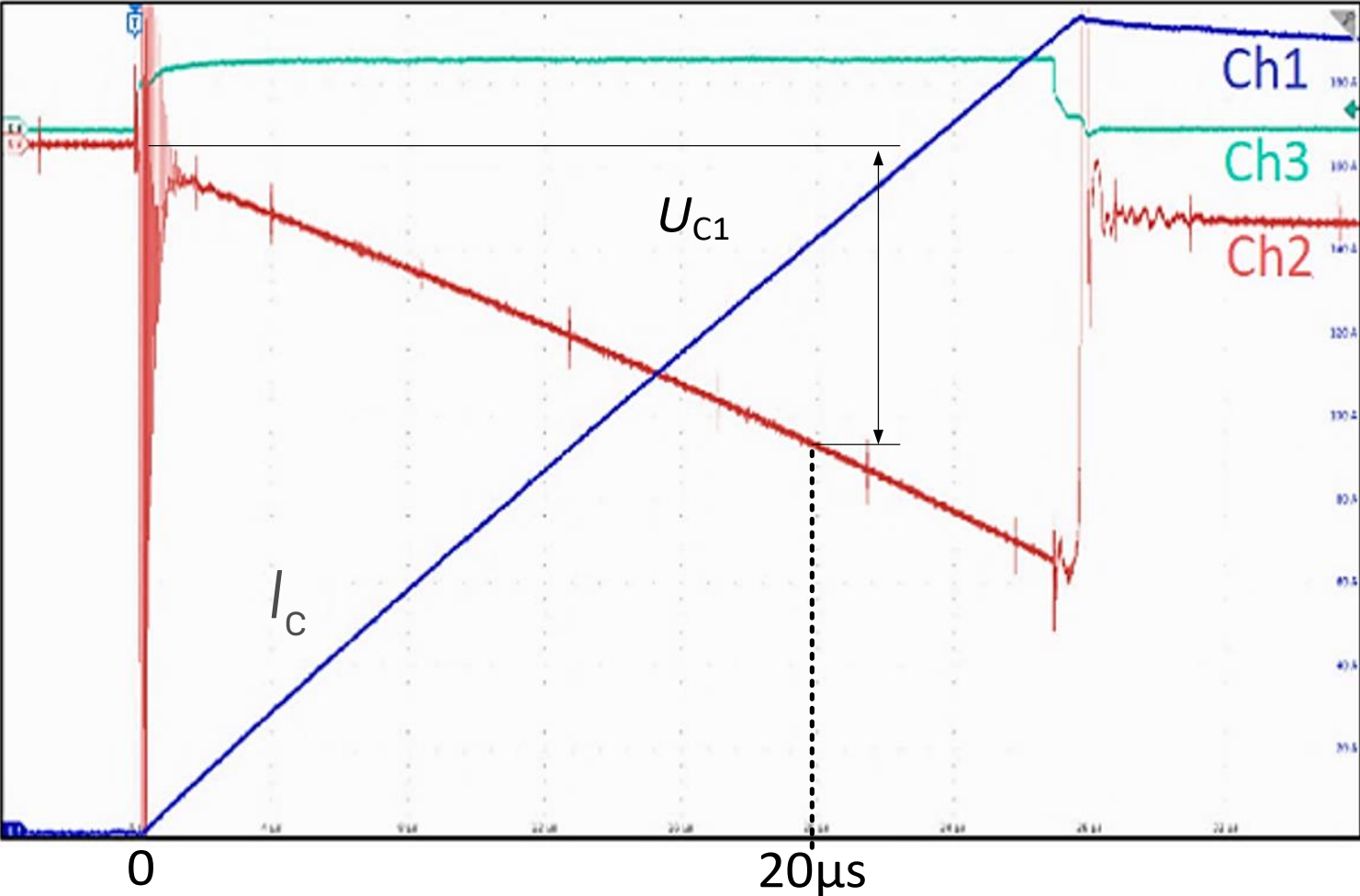


	Variant 1	Variant 2	Variant 3
U_{C1} [V]	0,717	0,750	0,758
U_{C2} [V]	0,701	0,696	0,715
U_{C3} [V]	0,702	0,715	0,730
U_{C4} [V]	0,699	0,727	0,728
U_{C5} [V]	0,700	0,751	0,748
U_{C6} [V]	0,707	0,713	0,709
U_{C7} [V]	0,706	0,698	0,712
U_{C8} [V]	0,685	0,695	0,705

6. ROM Model validation - summary


Variant 1

 

Variant 2

 


Variant 3

 


	Variant 1	Variant 2	Variant 3
I_{C1} [A]	32,45	33,65	34,44
I_{C2} [A]	33,14	33,93	34,54
I_{C3} [A]	33,68	34,69	35,00
I_{C4} [A]	32,96	33,75	34,23
I_{C5} [A]	36,11	36,77	37,19
I_{C6} [A]	34,76	35,53	36,09
I_{C7} [A]	34,52	35,24	35,93
I_{C8} [A]	34,57	35,23	35,70

 
11% higher current for C_5 in compare to C_1



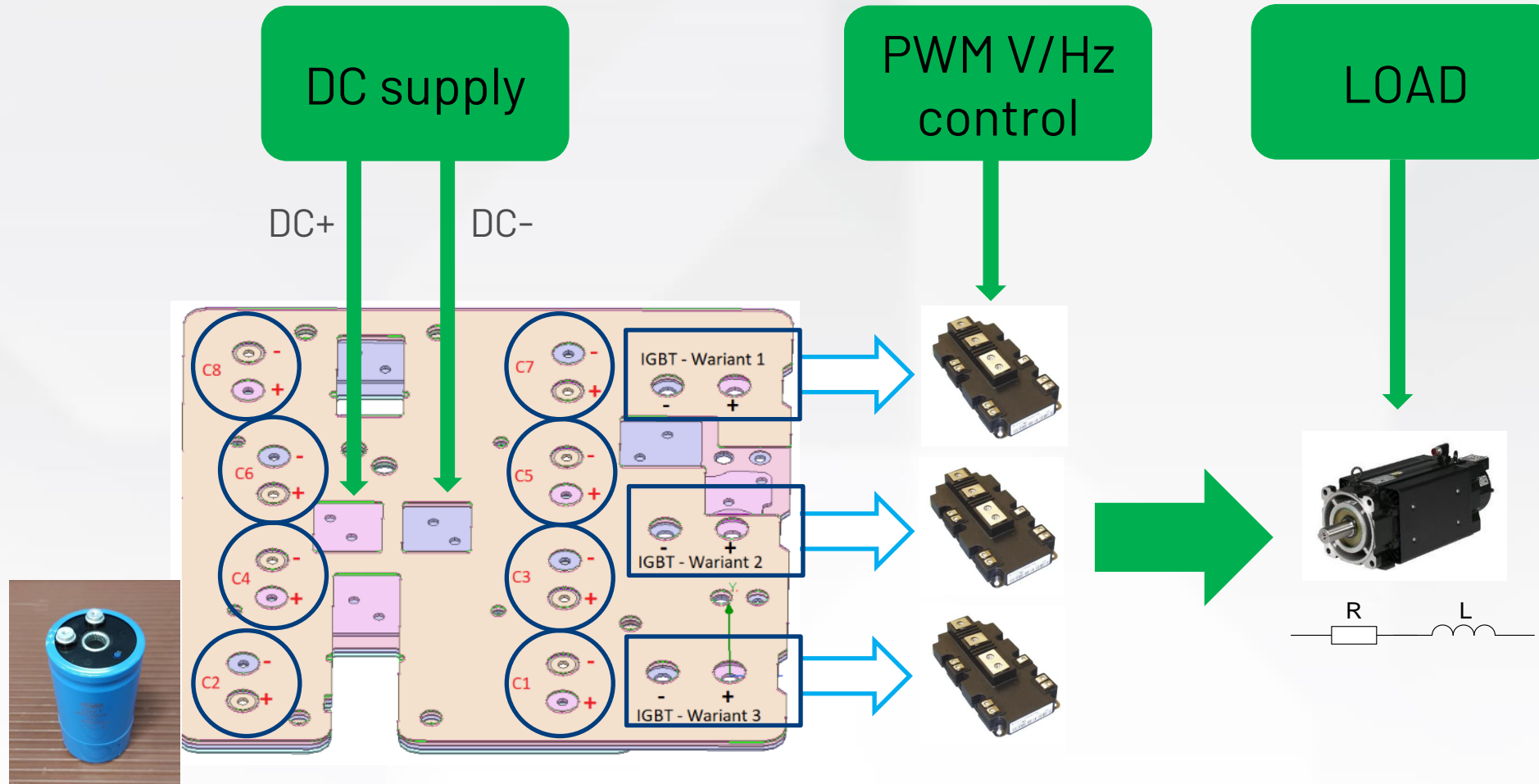7. DC/AC inverter simulations with busbar ROM model




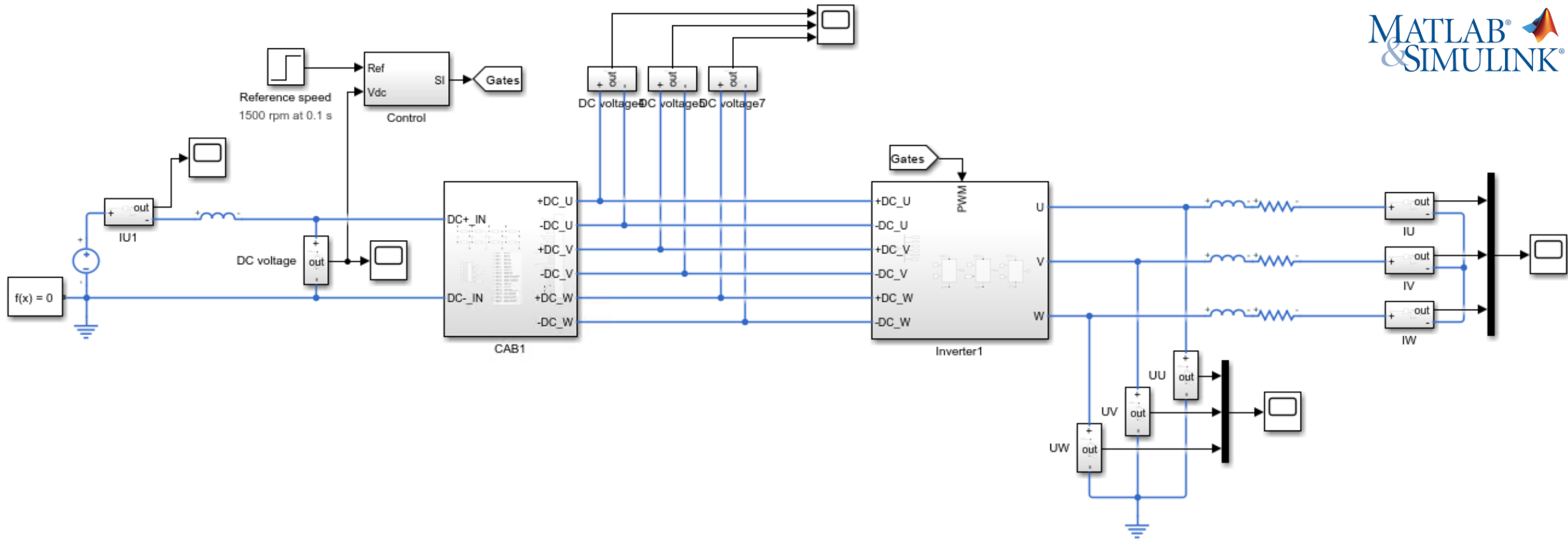7. DC/AC inverter simulations with busbar ROM model – Simscape model




7. DC/AC inverter simulations with busbar ROM model – Simscape model




CAB1

 


- * node 1 MID:C2
- * node 2 MID:C3
- * node 3 MID:C5
- * node 4 MID:C8
- * node 5 MID:C10
- * node 6 MID:C11
- * node 7 MID:C13
- * node 8 MID:C16
- * node 9 MINUS:C4
- * node 10 MINUS:C6
- * node 11 MINUS:C12
- * node 12 MINUS:C14
- * node 13 MINUS:INPUT_MINUS
- * node 14 MINUS:T1_Output
- * node 15 MINUS:T2_Output
- * node 16 MINUS:T3_Output
- * node 17 PLUS:C1
- * node 18 PLUS:C7
- * node 19 PLUS:C9
- * node 20 PLUS:C15
- * node 21 PLUS:INPUT_PLUS
- * node 22 PLUS:T1_Input
- * node 23 PLUS:T2_Input
- * node 24 PLUS:T3_Input
- * node 25 MID:SinkMid
- * node 26 MINUS:SinkMinus
- * node 27 PLUS:SinkPlus

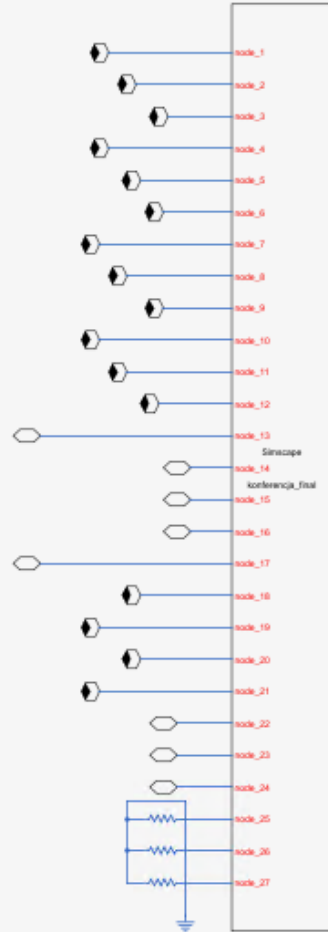

INVERTER1

  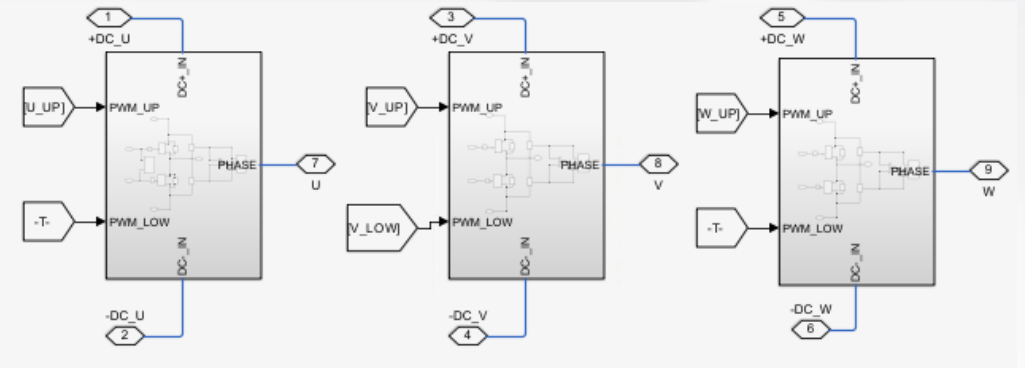

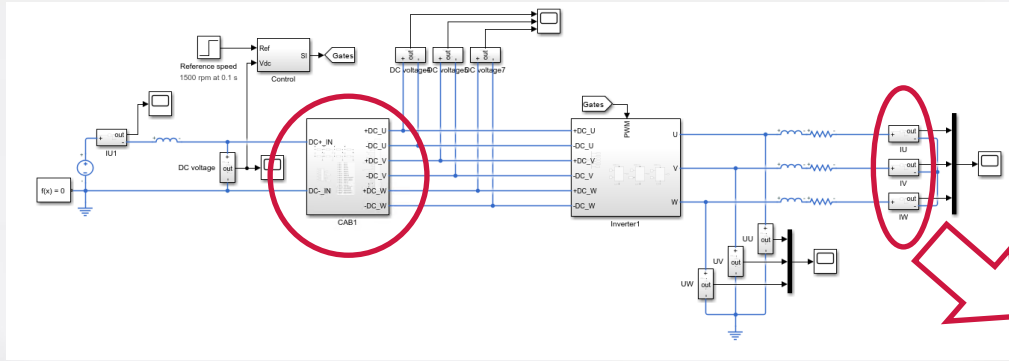
7. DC/AC inverter simulations with busbar ROM model – simulation results




Steady state, 1.9s to 2.0s
2h25m of simulation

Output currents

~354 A_{RMS}

 

Capacitors currents


 


10ms

100ms



7. DC/AC inverter simulations with busbar ROM model – simulation results

Capacitors current	
I_{C1} [A]	35,3
I_{C2} [A]	35,9
I_{C3} [A]	36,1
I_{C4} [A]	36,8
I_{C5} [A]	37,2
I_{C6} [A]	36,4
I_{C7} [A]	37,1
I_{C8} [A]	36,3

 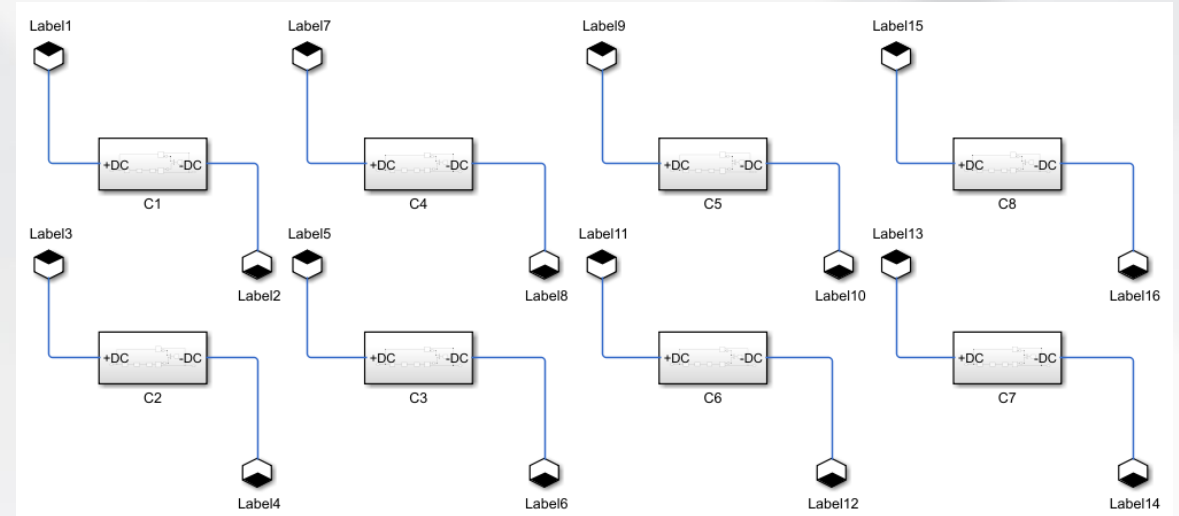

7. DC/AC inverter simulations with busbar ROM model – simulation results

Capacitors current	
I_{C1} [A]	35,3
I_{C2} [A]	35,9
I_{C3} [A]	36,1
I_{C4} [A]	36,8
I_{C5} [A]	37,2
I_{C6} [A]	36,4
I_{C7} [A]	37,1
I_{C8} [A]	36,3

  

	Variant 1	Variant 2	Variant 3	Mean
I_{C1} [A]	32,45	33,65	34,44	33,5
I_{C2} [A]	33,14	33,93	34,54	33,9
I_{C3} [A]	33,68	34,69	35,00	34,5
I_{C4} [A]	32,96	33,75	34,23	33,6
I_{C5} [A]	36,11	36,77	37,19	36,7
I_{C6} [A]	34,76	35,53	36,09	35,5
I_{C7} [A]	34,52	35,24	35,93	35,2
I_{C8} [A]	34,57	35,23	35,70	35,2

8. Summary & future research

Presented methodology demonstrates significant potential to be used during capacitor bank design or optimization for extended product lifetime

- Busbar layout has big impact on current sharing
- Detailed capacitors parameters should be considered
- Possibility to determine currents flowing through each capacitor

Methodology improvement needed:

- Temperature impact on current sharing
- Comparison of different available measurement method for capacitor parameters

Simulation tools

- MATLAB/Simulink environment allows for simple and transparent way of importing .cir model from Ansys environment,
- Busbar ROM models can be used to build more advanced multiphysics simulation models
- Model optimization required to speed-up simulation time



**Rockwell
Automation**

expanding **human possibility**[®]



www.rockwellautomation.com

